

List of components

| | | | | | | |
|-----------------|------------------|----------------|------|---|--------------------------------------|----------------|
| C ₁ | = 8,2 pF | 50 V | | R ₁₀ | = 12 K Ω | ¼W |
| C ₂ | = 10 μ F | 16 V | | R ₁₁ | = 680 Ω | ¼W |
| C ₃ | = 33 μ F | 16 V | | R ₁₂ | = 2,2 K Ω | ¼W |
| C ₄ | = 33 pF | 50 V | N750 | R ₁₃ | = 100 Ω | 2W |
| C ₅ | = 10 nF | 50 V | | R ₁₄ | = 100 Ω | 2W |
| C ₆ | = 100 nF | 50 V | | R ₁₅ | = 1,0 Ω | ½W |
| C ₇ | = 10 nF | 50 V | | R ₁₆ | = 12 K Ω | ¼W |
| C ₈ | = 10 nF | 50 V | | R ₁₇ | = 3,3 K Ω | ½W |
| C ₉ | = 27 pF | 50 V | N750 | R ₁₈ | = 10 Ω | 2W |
| C ₁₀ | = 10 nF | 50 V | | R ₁₉ | = 10 Ω | 2W |
| C ₁₁ | = 100 nF | 50 V | | R ₂₀ | = 10 Ω | 2W |
| C ₁₂ | = 10 nF | 50 V | | R ₂₁ | = 100 Ω | 2W |
| C ₁₃ | = 100 pF | 50 V | N750 | R ₂₂ | = 47 Ω | 2W |
| C ₁₄ | = 3 x 470 pF | 50 V | N750 | R ₂₃ | = 27 Ω | 2W |
| C ₁₅ | = 47 nF | 50 V | | R ₂₄ | = | |
| C ₁₆ | = 180 pF | 500 V | N750 | R ₂₅ | = 120 Ω | 2W |
| C ₁₇ | = 180 pF | 500 V | N750 | R ₂₆ | = 10 Ω | ½W |
| C ₁₈ | = 47 nF | 50 V | | R ₂₇ | = 10 Ω | ½W |
| C ₁₉ | = 100 pF | 500 V | N750 | R ₂₈ | = 120 Ω | 2W |
| C ₂₀ | = 47 pF | 500 V | N750 | R ₂₉ | = Trimmer | 220 K Ω |
| C ₂₁ | = 100 nF | 50 V | | R ₃₀ | = 47 K Ω | ¼W |
| C ₂₂ | = 100 nF | 50 V | | R ₃₁ | = 27 Ω | ½W |
| C ₂₃ | = 33 pF | 50 V | N750 | R ₃₂ | = 3,3 K Ω | ¼W |
| C ₂₄ | = 2,2 pF | 50 V | N750 | R ₃₃ | = 1,2 K Ω | ¼W |
| C ₂₅ | = 3,3 pF | 50 V | N750 | R ₃₄ | = 3,9 K Ω | ¼W |
| C ₂₆ | = 100 nF | 50 V | | R ₃₅ | = 330 Ω | ¼W |
| C ₂₇ | = 100 nF | 50 V | | R ₃₆ | = 2,2 K Ω | ¼W |
| C ₂₈ | = 100 nF | 50 V | | R ₃₇ | = 9 turns ϕ 6 mm resistive wire | |
| C ₂₉ | = 4700 μ F | 50 V | | R ₃₈ | = 470 Ω | ¼W |
| C ₃₀ | = 4700 μ F | 50 V | | R ₃₉ | = 3,3 K Ω | ¼W |
| C ₃₁ | = 2200 μ F | 50 V | | R ₄₀ | = 330 Ω | ¼W |
| C ₃₂ | = 100 nF | 50 V | | R ₄₁ | = 330 Ω | ¼W |
| C ₃₃ | = 100 nF | 50 V | | R ₄₂ | = 82 K Ω | ¼W |
| C ₃₄ | = 2,2 μ F | 16 V | | R ₄₃ | = 56 K Ω | ¼W |
| C ₃₅ | = 470 pF | 50 V | | R ₄₄ | = 330 Ω | 2W |
| C ₃₆ | = 150 pF | 50 V | | D ₁ = D ₂ = D ₁₀ = D ₁₁ = D ₁₂ | = 1N4148 | |
| C ₃₇ | = 2,2 μ F | 16 V | | D ₃ = D ₄ = D ₆ = D ₇ = D ₈ = D ₉ | = 1N4004 | |
| C ₃₈ | = 100 nF | 50 V | | D ₅ | = Zener 12 V 1W | |
| C ₃₉ | = 470 nF | 63 V ~ | | D ₁₃ | = Zener 7,5 V ½W | |
| R ₁ | = 18 Ω | ½W | | D ₁₄ | = 1N5400 | |
| R ₂ | = 470 Ω | ¼W | | P | = Bridge 60 V 25 A | |
| R ₃ | = 56 K Ω | ¼W | | Tr ₁ = Tr ₂ | = BF 245 | |
| R ₄ | = 22 K Ω | ¼W | | Tr ₃ = Tr ₅ = Tr ₁₀ | = BC 547 | |
| R ₅ | = 180 Ω | ¼W | | Tr ₄ | = BC 337 | |
| R ₆ | = Trimmer | 4,7 K Ω | | Tr ₆ | = BD 179 | |
| R ₇ | = 4,7 K Ω | ¼W | | Tr ₇ = Tr ₈ | = MRF422 | |
| R ₈ | = 330 Ω | 2W | | Tr ₉ | = TIP 142 | |
| R ₉ | = 1,2 K Ω | ½W | | Ic ₁ | = LM 7824 | |